 


Very High Speed Integrated Circuits Hardware Description Language


Lesson 3 VHDL Registers



Lesson 3 outline


- Multiplex and demultiplex (Chapter 6)
- Tri state (Chapter 7)
- Flip-flops and registers (Chapter 8)

Multiplexer “when else”

 

```
Mux_out <=A WHEN Mux_Control =‘0’  
      ELSE Mux_out <=B;
```

Multiplexer “if”

 

```
Process(A,B,Mux_control)
```


```
begin
```

```
  if Mux_control = '0' then Mux_out <= A
```

```
    else Mux_out <= B; end if;
```

```
end process;
```

Multiplexer “case”

 

```
Process(A,B,Mux_control)
```

```
Begin
```

```
case Mux_control is
```

```
when '0' =>
```

```
    mux_out <= A;
```

```
when '1'=>
```

```
    mux_out <= B;
```

```
when others =>
```


```
    mux_out <= A;
```

```
end case;
```

```
end process;
```

```
end
```

Tri-State

 

ENTITY tristate IS

PORT(A,Control : IN STD_LOGIC;

Tri_out :INOUT STD_LOGIC);

END tristate;

Tri-State 2

ARCHITECTURE behaviour OF tristate IS

BEGIN

Tri_out <= A WHEN Control ='0' ELSE 'Z';

END behaviour;

FLIP FLOPS

In VHDL you have many possibilities to implement flipflops.

The different ff as jk and rs can also be implemented.

However, most of the time when using FPGA, d-ff are already implemented.

Therefore we always use d-ff.

D- FF

*-- Positive edge triggered D flip-flop
-- If WAIT is used no sensitivity list is used*

PROCESS

BEGIN

WAIT UNTIL (Clock'EVENT AND

Clock='1');

Q1 <= D;

END PROCESS;

Gated D- FF

```
PROCESS (Reset,Clock)
BEGIN
    IF reset = '1' THEN
        Q4 <= '0';
    ELSIF (clock'EVENT AND clock='1') THEN
        IF Enable = '1'
            THEN Q4 <= D;
        END IF;
    END IF;
END PROCESS;
```

Gated D-FF registered

```
PROCESS (Reset,Clock)
  BEGIN
    IF reset = '1' THEN
      Q4 <= '00000000';
    ELSIF (clock'EVENT AND clock='1') THEN
      IF Enable = '1'
        THEN Q4 <= D;
      END IF;
    END IF;
  END PROCESS;
```

Case statement

```
process(a)
begin
    case a is
        when "00" => b <= "1000";
        when "01" => b <= "0100";
        when "10" => b <= "0010";
        when "11" => b <= "0001";
        when others => report
            "unreachable" severity    failure;
    end case;
end process
```

Assignments

- **Do self test chapter 7,8**
- **Do the exercises chapter 6,7,8**