 


Very High Speed Integrated Circuits Hardware Description Language

Lesson 2 VHDL Synthesis




Lesson 2 outline

- Levels of design (synthesis)
- Behavioural
- Structural
- Register Level
- Timing (chapter4)
- Seven segment decoder
(chapter 5)
- Questions.

Behavioral level

```
behavior OF ilatch IS
  BEGIN
    PROCESS (A, B)
      BEGIN
        IF A = '0' THEN
          Output1 <= '0';
          Output2 <= '0';
        ELSE
          IF B = '1' THEN
            Output1 <= '1';
            Output2 <= '1';
          ELSE
            Output1 <= '0';
          END IF;
        END IF;
      END PROCESS;
    END behavior;
```

Structural level

 

architecture structural of BUZZER is

component AND2

port (in1, in2: in std_logic;
out1: out std_logic);

end component;

component OR2

port (in1, in2: in std_logic;
out1: out std_logic);

end component;

component NOT1

port (in1: in std_logic;
out1: out std_logic);

end component;

signal DOOR_NOT, SBELT_NOT, B1, B2: std_logic;

begin

U0: NOT1 port map (DOOR, DOOR_NOT);

U1: NOT1 port map (SBELT, SBELT_NOT);

U2: AND2 port map (IGNITION, DOOR_NOT, B1);

U3: AND2 port map (IGNITION, SBELT_NOT, B2);

U4: OR2 port map (B1, B2, WARNING)

end structural;

RTL level design

**BEHAV_DFF of DFF_CLEAR is
Begin**

```
DFF_PROCESS: process (CLK, CLEAR)  
begin  
    if (CLEAR = '1') then  
        Q <= '0';  
    elsif (CLK'event and CLK = '1') then  
        Q <= D;  
    end if;  
    end process;  
end BEHAV_DFF;
```

level descriptions

ARCHITECTURE behavior OF gate_network IS

BEGIN

X <= A AND NOT(B OR C) AND (D(1) XOR D(2)) after 10 ns;

PROCESS (A,B,C,D)

BEGIN

Y <= A AND NOT(B OR C) AND (D(1) XOR D(2))after 20 ns;

END PROCESS;

END behavior;

Explicit processes, The Sensitivity list

```
compute_xor: process (b,c)  
begin  
a<=b xor c;  
end process
```

```
compute_xor: process (c)  
begin  
a<=b xor c;  
end process;
```



Implicit processes

In implicit processes you do not see the word “process”. Each assignment is a process on itself

Example:

```
begin  
  a<=b xor c;  
  d<=b and c;  
end archx;
```


7 segments decoder

  

7 segments decoder

Architecture with case statement

ARCHITECTURE behaviour OF sevensegm

PROCESS(msd)

BEGIN

CASE msd IS

WHEN "0000" =>

msd_7seg <= "1111110";

WHEN "0000" =>



msd_7seg <="0110000";

etc

Assignment 1, 2

Write a structural architecture of the next schematics:

Exclusive OR (XOR)

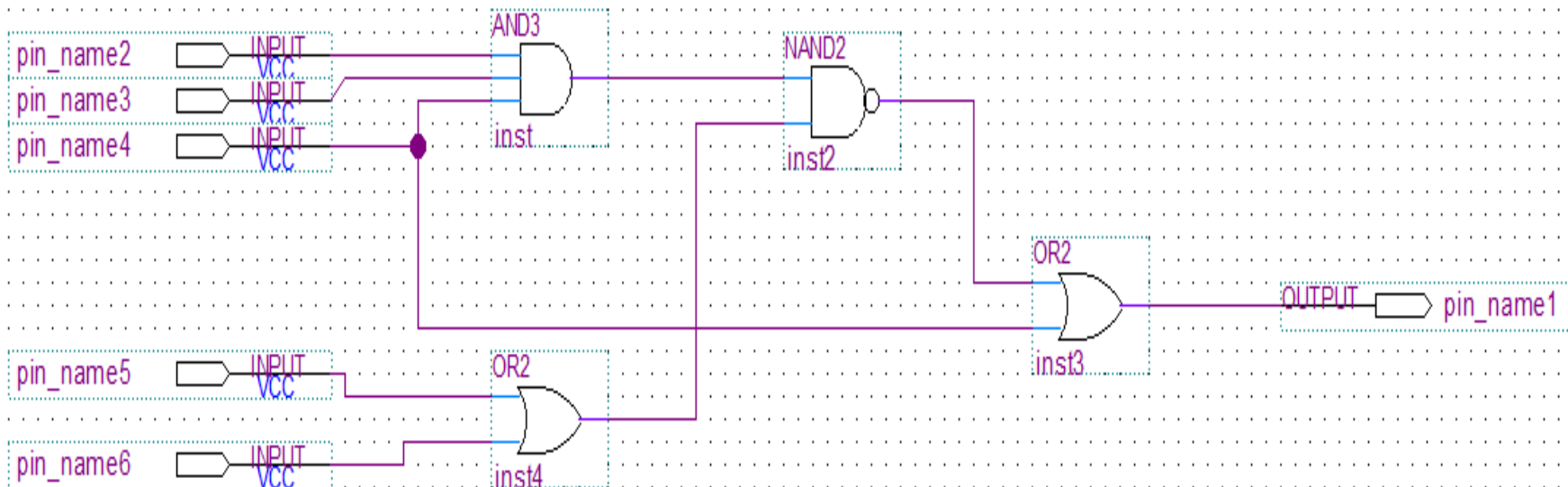 

Assignment 3

Draw the schematic of the vhdl description: See also next page

```
architecture structural_2 of multiplexer_4_to_1_st is  
component
```

```
  NOT1 port( in1 : in std_logic; out1 : out std_logic);  
end component;
```

```
component
```

```
  AND3 port( in1, in2, in3 : in std_logic; out1 : out std_logic);  
end component;
```

```
component
```

```
  OR4 port( in1, in2, in3, in4 : in std_logic; out1 : out std_logic);  
end component;
```

Assignment 4

Write an alternative in behavioural VHDL

```
signal S_n : std_logic_vector(0 to 1);  
signal N : std_logic_vector(0 to 3);  
  
begin  
  g0: NOT1 port map (S(0), S_n(0));  
  g1: NOT1 port map (S(1), S_n(1));  
  g2: AND3 port map (S_n(1), S_n(0), D(0), N(0));  
  g3: AND3 port map (S_n(1), S(0), D(1), N(1));  
  g4: AND3 port map (S(1), S_n(0), D(2), N(2));  
  g5: AND3 port map (S(1), S(0), D(3), N(3));  
  g6: OR4 port map (N(0), N(1), N(2), N(3), Y);  
end structural_2;
```

Exercises (week 2)

- Do the self test of chapter 3, 4, 5
- Read chapter 3, 4, 5
- Prepare the practical work of chapter 3 ,4 and 5

Submit before week 4 in Black Board:
practical work and the self tests in one file.
.pdf or word